


# CS-230 Project

## Datapaths

1) ADD: add  $r_c, r_a, r_b$




$r_c = r_a + r_b$  &  $GZ$  modifies.

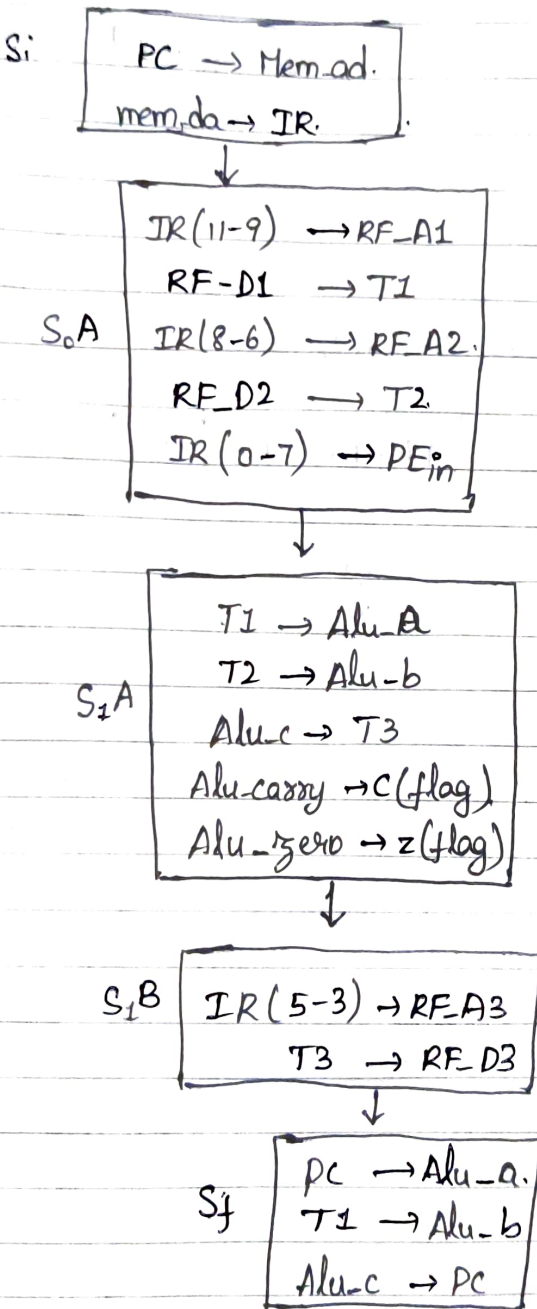


② ADC: adc  $r_c, r_a, r_b$ .

00-01	RA	RB	RC	0	10
-------	----	----	----	---	----


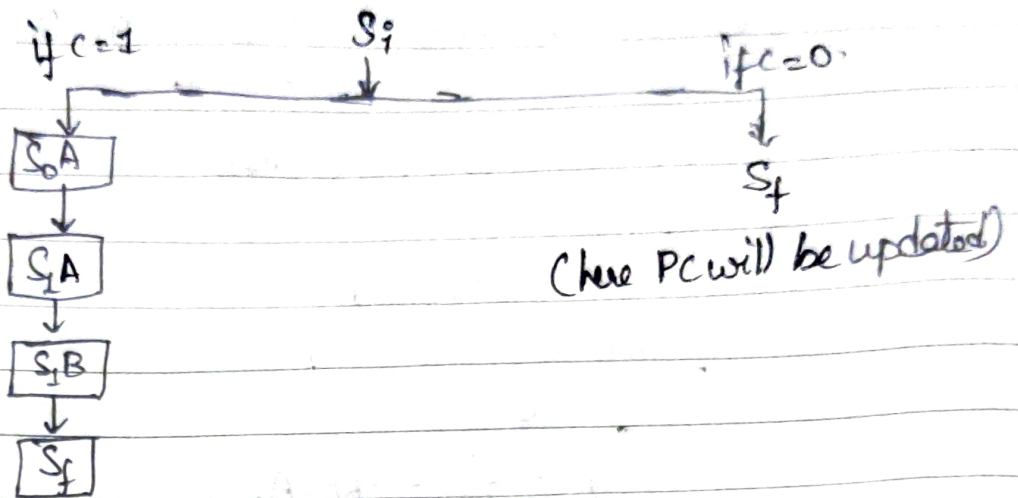


③ ADZ: adz  $r_c, r_a, r_b$ .



00-01	RA	RB	RC	0	01
-------	----	----	----	---	----

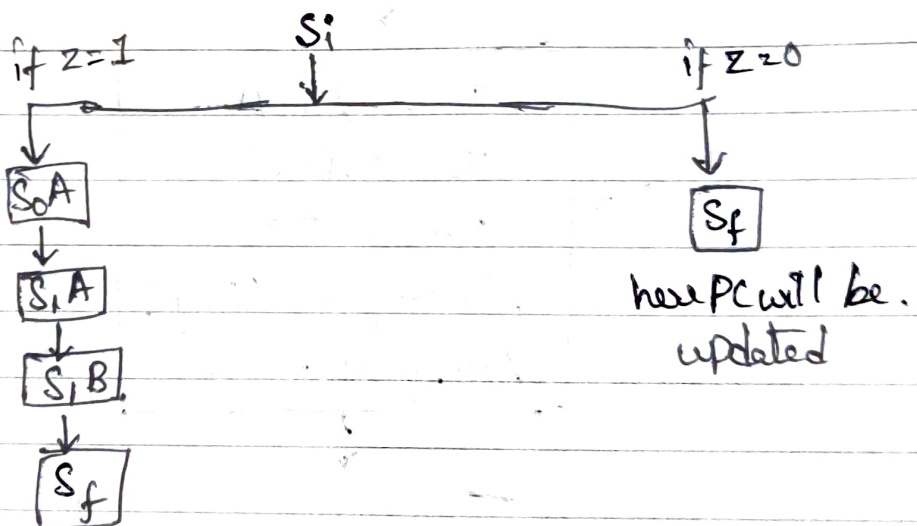

④ ADL:  $\text{Adl } r_c, r_a, r_b.$

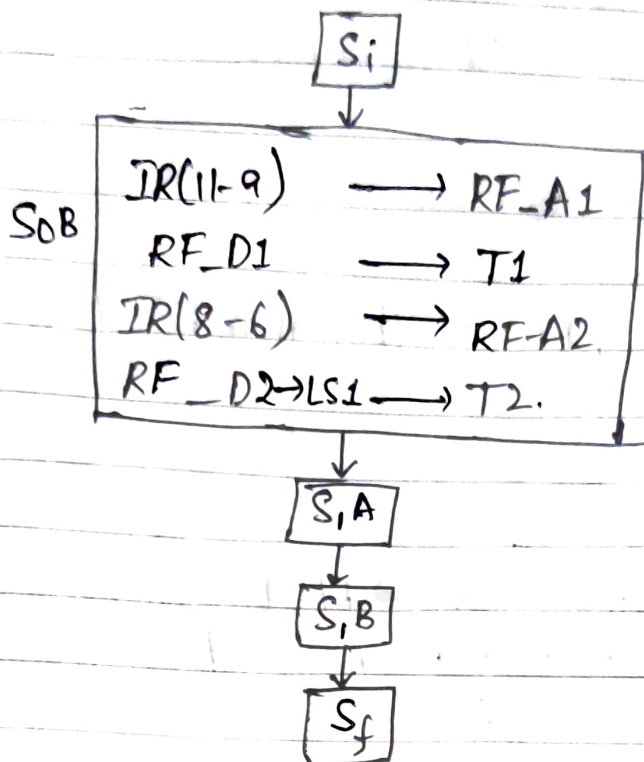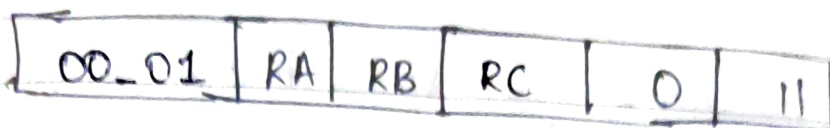

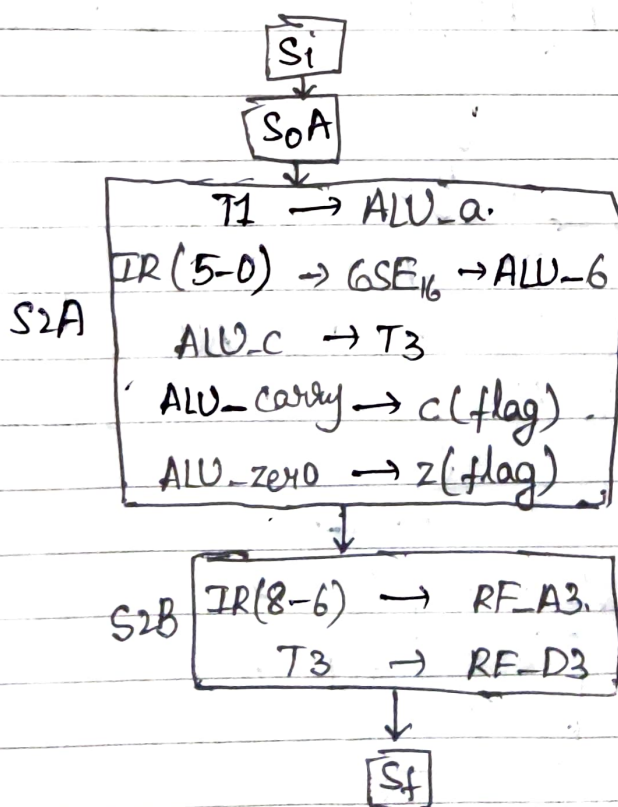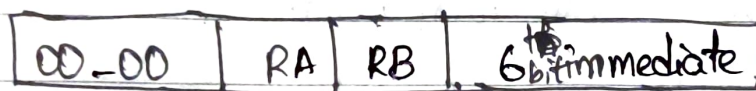
⑤ ADI:  $\text{adi } r_b, r_a, \text{imm6}$





6) NDU : ndu  $\cdot r_c, r_a, r_b$ .

→ similar as add instruction but the operation in ALU is nand which is decided by alu-control. Similarly for NDC and NDZ

9) LHI : lhi  $r_a, Imm$


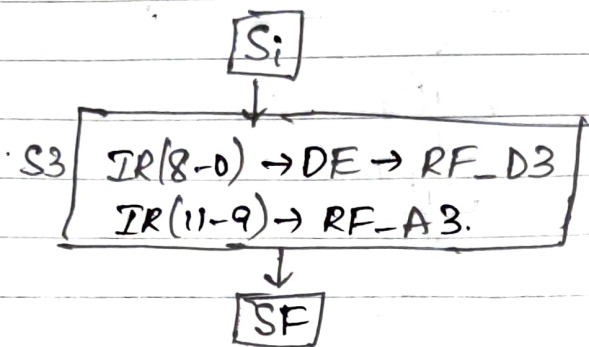


10) LW : Lw  $r_a, r_b, Imm$

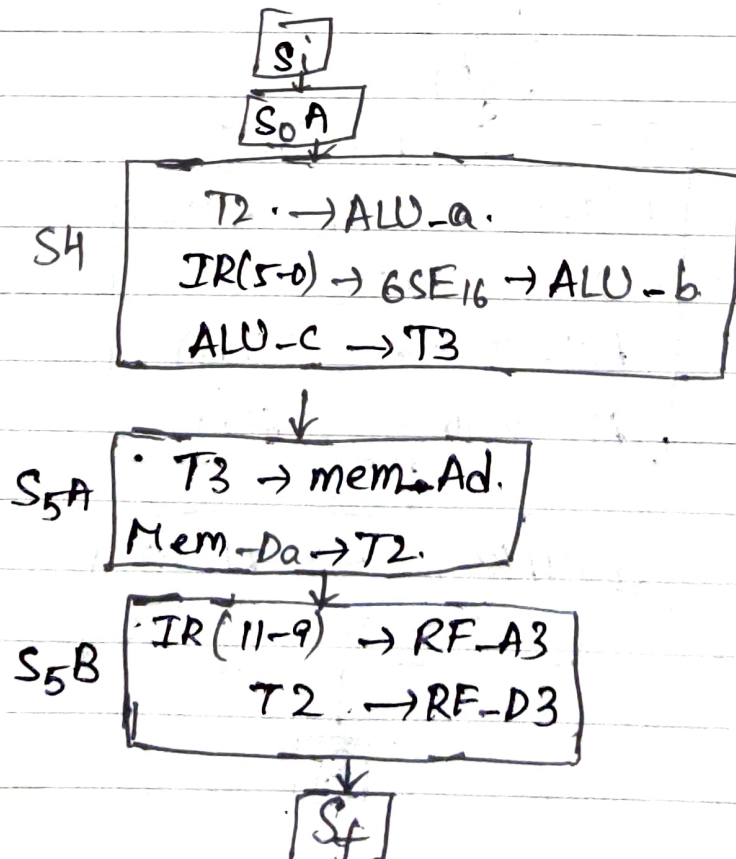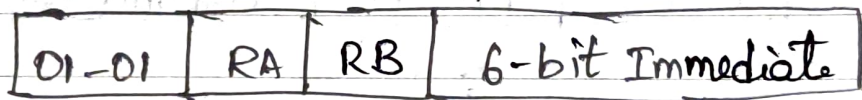


11)

SW : Sw Ya, Yb, Imm.

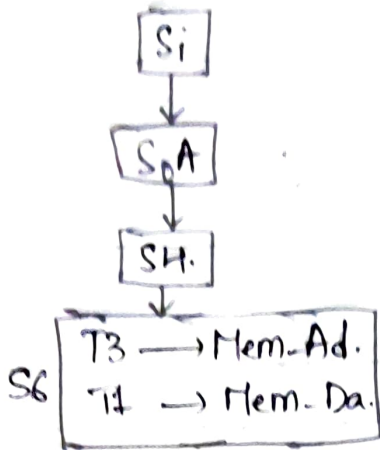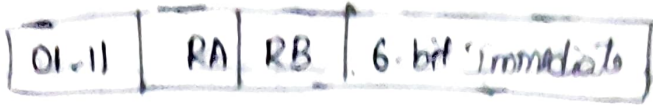


12)

LM : L Ya, Imm

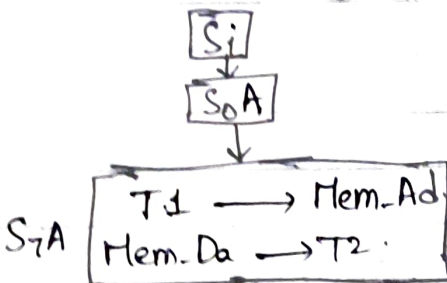

PE=1

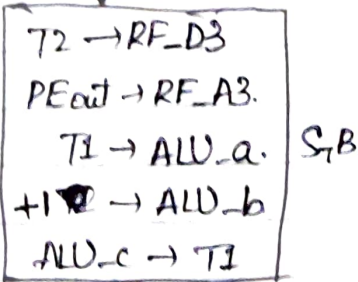

S7A

Sf


PE=0

Sf will be updated PC




(13)

SM : Sm @ Ya, Imm


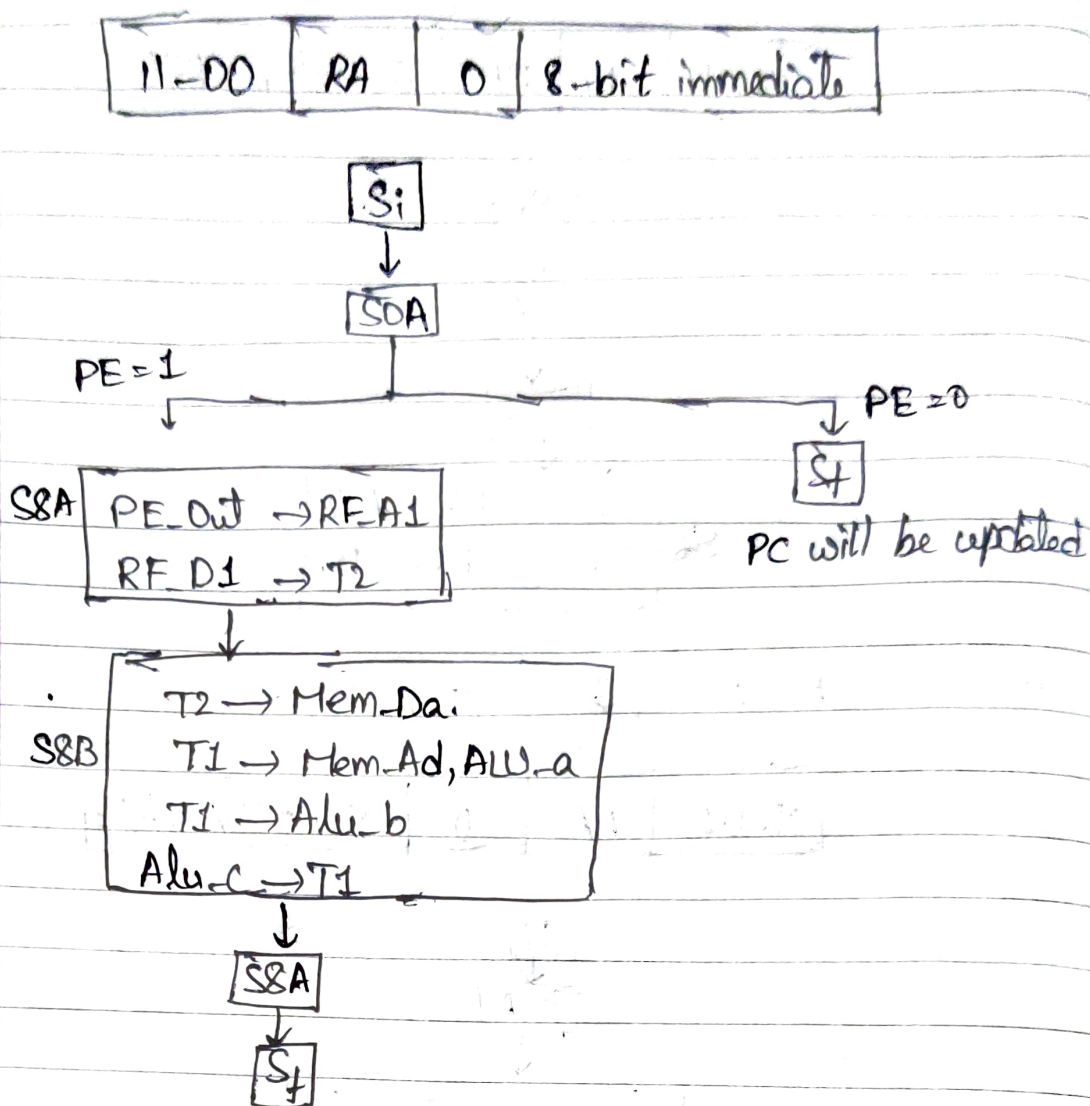


(14)



BEQ : Beq ra, rb, Imm.

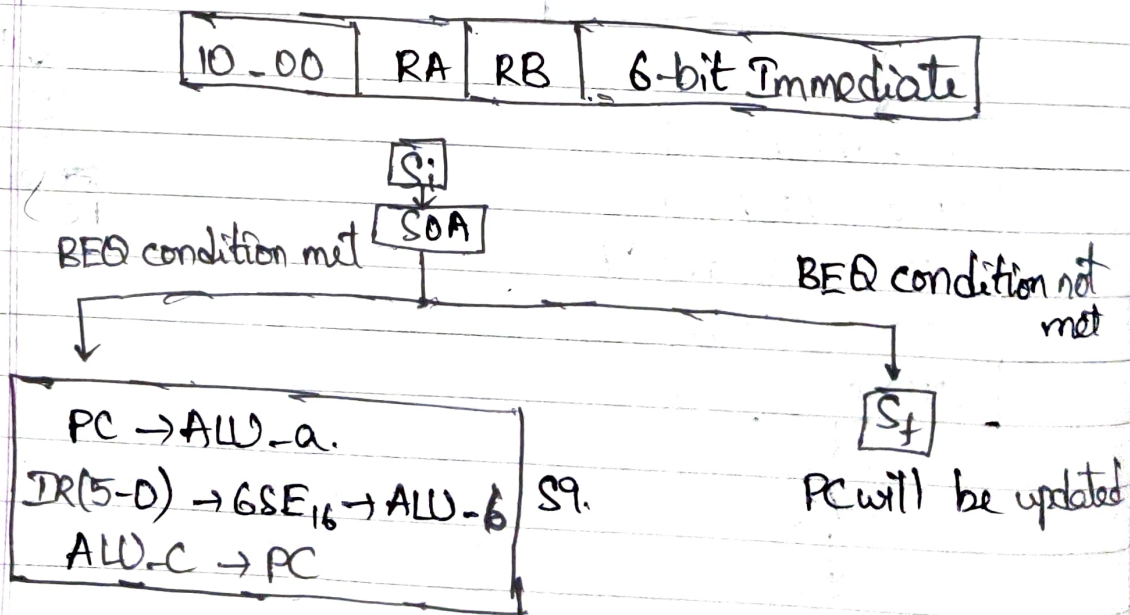


⑮ JAL : jalr  $r_a, Imm$

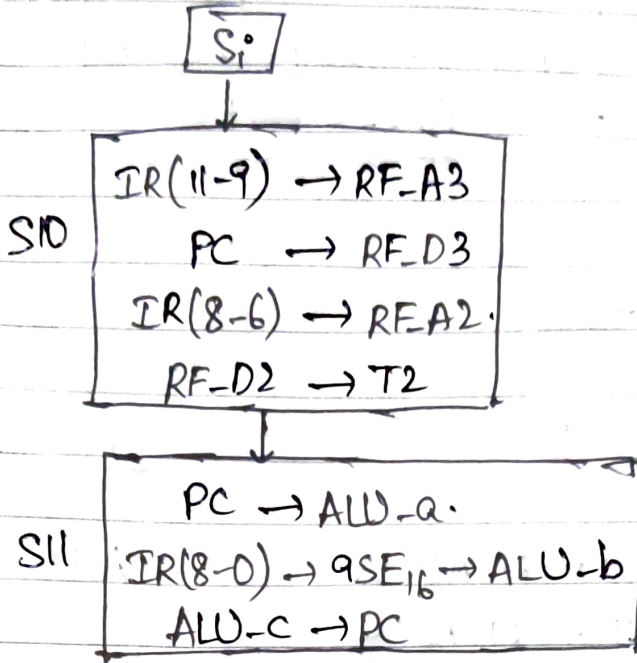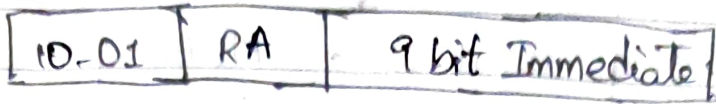


⑯ JLR : jalr  $r_a, r_b$

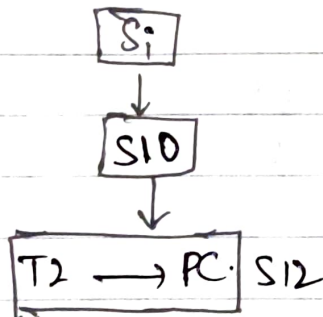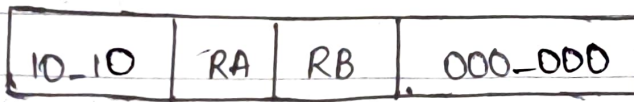

⑰ JRI : jri  $r_a, Imm$

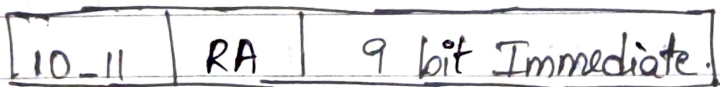

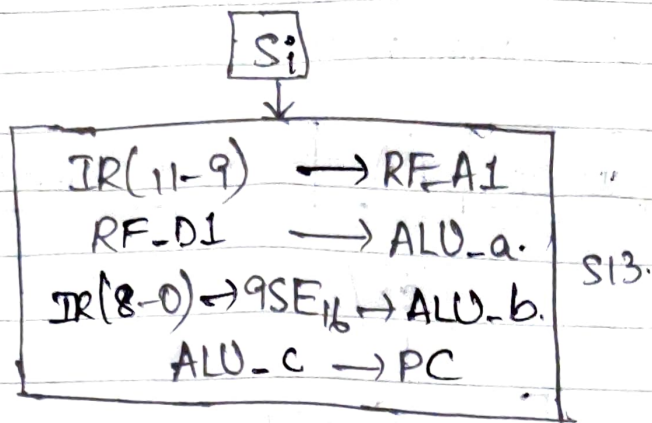

### Connections:-

RE-A1: (M1)

IR(11-9)  $\rightarrow$  RE-A1 0  
PE-Out  $\rightarrow$  RE-A1 1

PC: (M4)

ALU-c  $\rightarrow$  PC 0  
T2  $\rightarrow$  PC 1

RE-A2:

IR(8-6)  $\rightarrow$  RE-A2.

T1: (M5)

RF-D1  $\rightarrow$  T1 0  
ALU-c  $\rightarrow$  T1 1

RE-A3: (M2)

IR(5-3)  $\rightarrow$  RE-A3 00  
IR(8-6)  $\rightarrow$  RE-A3 01  
IR(11-9)  $\rightarrow$  RE-A3 10  
PE-Out  $\rightarrow$  RE-A3 11

T2: (M6)

RF-D2  $\rightarrow$  T2 00  
RF-D2  $\rightarrow$  LSI  $\rightarrow$  T2 01  
RF-D1  $\rightarrow$  T2 10  
Mem-Da  $\rightarrow$  T2 11

RE-D3: (M3)

T3  $\rightarrow$  RE-D3 00  
IR(8-0)  $\rightarrow$  DE  $\rightarrow$  RE-D3 01  
T2  $\rightarrow$  RE-D3 10  
PC  $\rightarrow$  RE-D3 11

T3: (M7)

Mem-Da  $\rightarrow$  T3 0  
ALU-c  $\rightarrow$  T3 1

ALU-a: (M8)

T1  $\rightarrow$  ALU-a 00  
PC  $\rightarrow$  ALU-a 01  
T2  $\rightarrow$  ALU-a 10  
RF-D1  $\rightarrow$  ALU-a 11



ALU-b: (19)

T2 → ALU\_b 00

$T1 \rightarrow ALU\_b$       00  
 $2(5-A) : 1$       01

IR(5-0) → 6SE<sub>16</sub> → AW-6 01  
IR(8-0) → 8SE<sub>16</sub> → AW-6 10

IR(8-0)  $\rightarrow$  9SE<sub>16</sub>  $\rightarrow$  ALU-b 11

Mem-Da (H10)

T1 → Mem-Da 0

$T_2 \rightarrow \text{Mem-Da } 1$

Mem-Ad :


PC  $\rightarrow$  Mem-Ad 00

T3 → Mem. Ad 01

ALU - C  $\rightarrow$  Mem Ad 10

T1  $\rightarrow$  Mem\_Ad 11

## State Transition Diagram

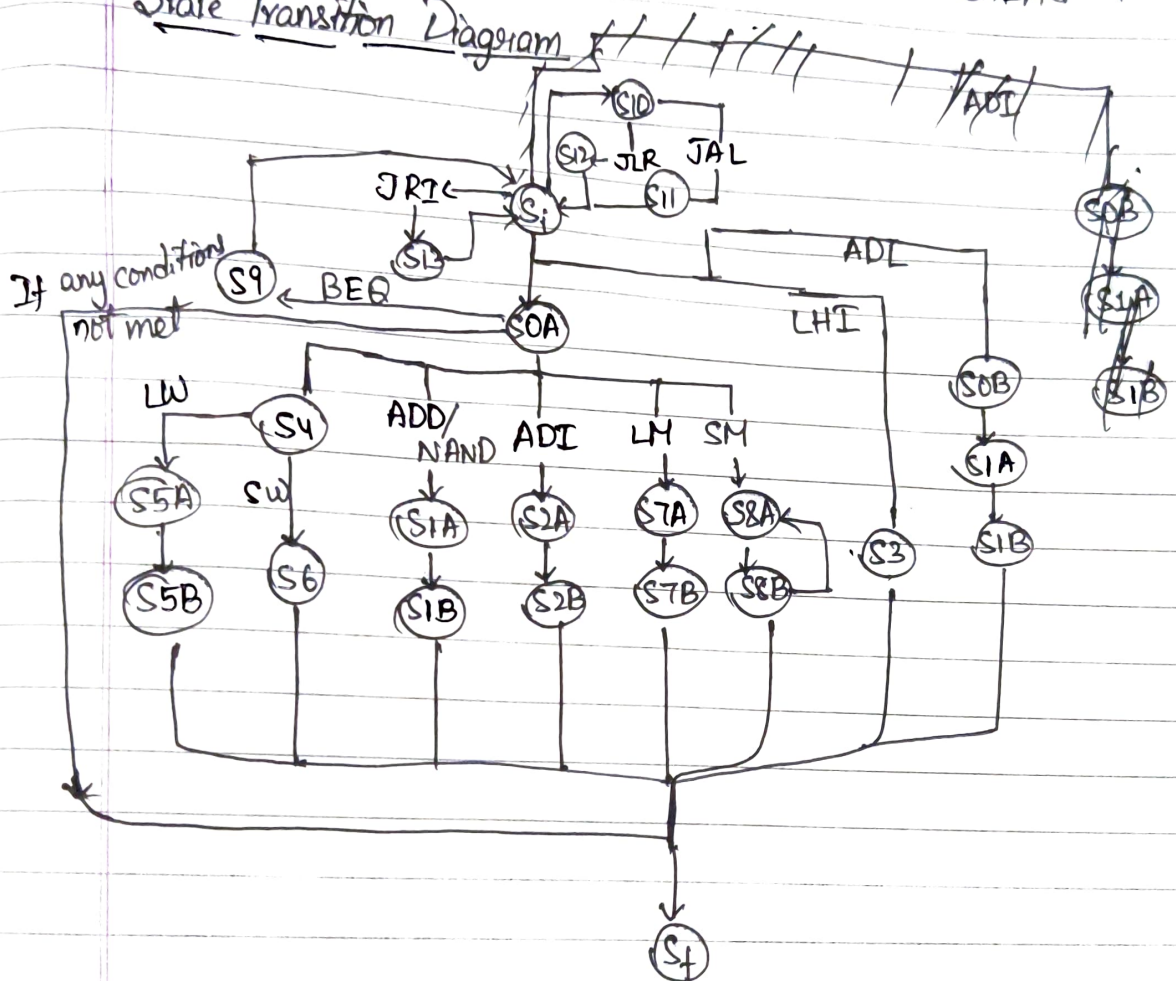

	W-PC	W-IR	W-Mem	W-RF	H1 (RF-A1)	H2 (RF-A3)	H3 (RF-D3)	H4 PC	H5 T1	H6 T2	H7 T3	H8 ALD-a	H9 ALL-b	H10 Mem-Da	H11 Mem-Ad
Si	0	1	0	0	x	00	xx	xx	x	xx	x	xx	xx	x	xx
SDA	0	0	0	0	0	xx	xx	xx	0	00	x	xx	xx	x	xx
SDB	0	0	0	0	0	xx	xx	xx	0	01	x	xx	xx	x	xx
S1A	0	0	0	0	x	xx	xx	xx	x	xx	1	00	00	x	xx
S1B	0	0	0	0	x	00	00	xx	x	xx	x	00	00	x	xx
S2A	0	0	0	0	x	xx	xx	xx	x	xx	x	xx	xx	x	xx
S2B	0	0	0	0	x	010	00	xx	x	xx	x	xx	xx	x	xx
S3	0	0	0	0	x	10	01	xx	x	xx	1	10	10	x	xx
S4	0	0	0	0	x	xx	xx	xx	x	xx	x	xx	xx	x	xx
S5A	0	0	0	1	x	10	10	xx	x	xx	x	xx	xx	x	xx
S5B	0	0	0	1	x	xx	xx	xx	x	xx	x	xx	xx	x	xx
S6	0	0	1	0	x	xx	xx	xx	x	xx	x	xx	xx	x	xx
S7A	0	0	0	0	x	xx	xx	xx	x	xx	x	xx	xx	x	xx
S7B	0	0	0	1	x	11	10	xx	x	xx	x	xx	01	x	xx
S8A	0	0	0	0	1	xx	xx	xx	x	xx	x	xx	01	x	xx
S8B	0	0	0	0	x	xx	xx	xx	x	xx	x	xx	01	x	xx
S9	0	0	0	0	0	xx	xx	xx	x	xx	x	xx	10	x	xx
S10	0	0	0	1	0	10	xx	xx	x	xx	x	xx	xx	x	xx
S11	0	0	0	0	x	xx	xx	xx	x	xx	x	xx	xx	x	xx
S12	0	0	0	0	x	xx	xx	xx	x	xx	x	xx	xx	x	xx
S13	0	0	0	0	x	xx	xx	xx	x	xx	x	xx	xx	x	xx
f	0	0	0	0	0	xx	xx	xx	x	xx	x	xx	xx	x	xx

